



Digital Systems Design

A Simple Computer Design


Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 7-1



Architecture of a Simple Computer System

 - Three main units
 - Processor (CPU)
 - Memory
 - Instruction and data
 - Input/Output hardware
 - Communicates with other devices
- CPU contains basic registers
 - PC – program counter
 - IR – instruction register
 - AC – accumulator
 - MAR – memory address register
 - MDR – memory data register




Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 7-2



Computer Programs and Instructions

 

- Instructions stored in memory according to a format determined by the processor designer
 - For the simple computer, the format is 16 bits
 - 8-bit opcode – to determine the instruction
 - 8-bit address – to determine the address of one of the operands for the instruction
 - 256 word x 16-bits/word memory




Basic Computer Instructions

Instruction Mnemonic	Operation Performed	Opcode Value
ADD address	AC \leq AC + contents of memory address	00
STORE address	Contents of memory address \leq AC	01
LOAD address	AC \leq contents of memory address	02
JUMP address	PC \leq address	03
JNEG address	IF AC < 0 THEN PC \leq address	04



Processor Fetch, Decode and Execute Cycle

 - The CPU
 - Reads instructions from memory
 - Decodes the instruction
 - Carries out the operation
- A state machine (the control unit) controls the operation sequencing
- Implementing the fetch/decode/execute cycle requires
 - Several register transfers
 - Several clock cycles




Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 7-5



Detailed View of Fetch/Decode/Execute

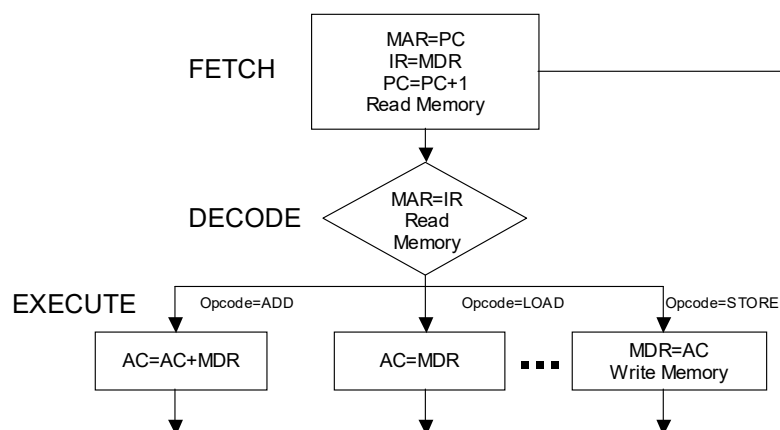


Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 7-6



Data Values at Reset

 - Reset forces the processor to a known state
- All registers will be cleared
- Since PC and MAR are reset to 00, the first instruction will be loaded from address 00




Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 7-7



 Example Instruction Execution (ADD)

- FETCH
 - MAR=PC prior to fetch
 - Read memory
 - IR=MDR
 - PC=PC+1
- After the memory access delay, the ADD instruction is available at the input to the IR
- At the same time, PC is incremented using a different bus
- In implementation, MAR=PC at the end of the fetch/decode/execute step
 - This saves a clock cycle in the FETCH step




Electrical & Computer Engineering

Dr. D. J. Jackson Lecture 7-8



 
Example Instruction Execution (ADD)

- DECODE
 - Decode opcode to determine next state
 - MAR=IR (low 8-bits)
 - Begin memory read
- Instructions are decoded in hardware using
 - Combinational logic
 - A small PLA
 - ROM
- When the address is clocked into the MAR, the data from memory will be available in the MDR



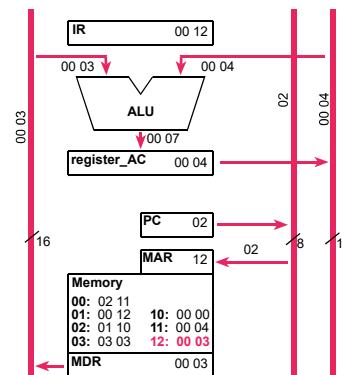Example Instruction Execution (ADD)

- EXECUTE
 - $AC = AC + MDR$
 - $MAR = PC^*$
 - GOTO FETCH
- The control unit has placed the processor in the execute state for the ADD instruction
 - Control signals for the ALU instruct it to perform an ADD instruction
- Depending on the complexity of the instruction, there could be multiple steps (sub-states) for an instruction
- * By setting $MAR = PC$ in every instruction's final execute state, a clock cycle can be saved in the FETCH state





VHDL Source Code

```
library ieee;
use      ieee.std_logic_1164.all;
use      ieee.numeric_std.all;

entity scomp is
generic( address_width  : integer := 8;
         data_width     : integer := 16);
port(

clock, reset                : in std_logic:= '1';
program_counter_out         : out std_logic_vector(address_width-1 downto 0);
register_ac_out              : out std_logic_vector(data_width-1 downto 0);
memory_data_register_out    : out std_logic_vector(data_width-1 downto 0);
memory_address_register_out : out std_logic_vector(address_width-1 downto 0);
memory_write_out            : out std_logic

);
end scomp;
```



VHDL Source Code

```
architecture rtl of scomp is
type ram is array(0 to 2 ** address_width-1) of unsigned(data_width-1 downto 0);
signal    ram_block : ram;
attribute ram_init_file : string;
attribute ram_init_file of ram_block : signal is "program.mif";

type scomp_fsm is ( reset_pc, fetch, decode, execute_add, execute_load,
                    execute_jneg,execute_jneg2, execute_store,
                    execute_store2, execute_jump );

signal state
signal instruction_register : scomp_fsm;
signal memory_data_register : unsigned(data_width-1 downto 0);
signal register_ac           : signed(data_width-1 downto 0);
signal program_counter       : unsigned(address_width-1 downto 0);
signal memory_address_register : unsigned(address_width-1 downto 0);
signal memory_write          : std_logic;
```



VHDL Source Code

```
begin
-- Output major signals
program_counter_out    <= std_logic_vector(program_counter);
register_AC_out         <= std_logic_vector(register_AC);
memory_data_register_out <= std_logic_vector(memory_data_register);
memory_address_register_out <= std_logic_vector(memory_address_register);
memory_write_out       <= memory_write;

process (clock)
begin
    if rising_edge(clock) then
        if (memory_write = '1') then
            ram_block(to_integer(memory_address_register)) <= unsigned(register_ac);
        end if;
        memory_data_register <= ram_block(to_integer(memory_address_register));
    end if;
end process;
```



VHDL Source Code

```
process (clock,reset)
begin
    if reset = '1' then
        state <= reset_pc;
    elsif rising_edge(clock) then
        case state is
            -- reset the computer, need to clear some registers
            when reset_pc =>
                program_counter <= (others => '0');
                register_ac <= (others => '0');
                state <= fetch;
            -- fetch instruction from memory and add 1 to pc
            when fetch =>
                instruction_register <= memory_data_register;
                program_counter <= program_counter + 1;
                state <= decode;
```



VHDL Source Code

```
-- decode instruction and send out address of any data operands
when decode =>
  case instruction_register( 15 downto 8 ) is
    when "00000000" =>
      state <= execute_add;
    when "00000001" =>
      state <= execute_store;
    when "00000010" =>
      state <= execute_load;
    when "00000011" =>
      state <= execute_jump;
    when "00000100" =>
      state <= execute_jneg;
    when others =>
      state <= fetch;
  end case;
-- execute the add instruction
when execute_add =>
  register_ac <= register_ac + signed(memory_data_register);
  state <= fetch;
```



VHDL Source Code

```
-- execute the store instruction
-- (needs two clock cycles for memory write and fetch mem setup)
when execute_store =>
  -- enable memory write, write register_ac to memory
  -- load memory address and data registers for memory write
  state <= execute_store2;

-- finish memory write operation and load memory registers
-- for next fetch memory read operation
when execute_store2 =>
  state <= fetch;

-- execute the load instruction
when execute_load =>
  register_ac <= signed(memory_data_register);
  state <= fetch;

-- execute the jump instruction
when execute_jump =>
  program_counter <= instruction_register(address_width-1 downto 0);
  state <= fetch;
```




VHDL Source Code

```
when execute_jneg =>
  if (register_ac < 0) then
    program_counter <= instruction_register(address_width-1 downto 0);
  end if;
  state <= execute_jneg2;
when execute_jneg2 =>
  state <= fetch;
when others =>
  state <= fetch;
end case;
end if;
end process;
```



VHDL Source Code

```
-- memory address register is already inside synchronous memory unit
-- need to load its value based on current state
-- (no second register is used - not inside a process here)

with state select
  memory_address_register <= (others => '0')
    when reset_pc,
    program_counter
    instruction_register(address_width-1 downto 0) when fetch,
    program_counter
    instruction_register(address_width-1 downto 0) when decode,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_add,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_store,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_store2,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_load,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_jump,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_jneg,
    program_counter
    instruction_register(address_width-1 downto 0) when execute_jneg2;

with state select
  memory_write <= '1' when execute_store,
                  '0' when others;
end rtl;
```



Example MIF File

```
DEPTH = 256;           % Memory depth and width are required      %
WIDTH = 16;             % Enter a decimal number                  %
ADDRESS_RADIX = HEX;   % Address and value radices are optional   %
DATA_RADIX = HEX;      % Enter BIN, DEC, HEX, or OCT; unless      %
CONTENT
BEGIN
[00..FF] :      0000;   % Range--Every address from 00 to FF = 0000 %
00       :      0210;   % LOAD AC with MEM(10) %
01       :      0011;   % ADD MEM(11) to AC %
02       :      0112;   % STORE AC in MEM(12) %
03       :      0212;   % LOAD AC with MEM(12) %
04       :      04FF;   % JNEG FF should jump to FFH %
05       :      0305;   % JUMP to 05 (loop forever) %
06       :      0306;   % JUMP to 06 (loop forever) %
10       :      AAAA;   % Data Value %
11       :      5555;   % Data Value %
12       :      0000;   % Data Value - should be FFFF after program %
FF       :      0306;   % JUMP to 06 %
END ;
```